

ASSIGNMENT 3

MADHU LATHA ADDANKI
madhulathaaddanki@gmail.com
FWC22129

IIT Hyderabad-Future Wireless Communication


April 2023

Contents


1 Problem

GATE EC-2020

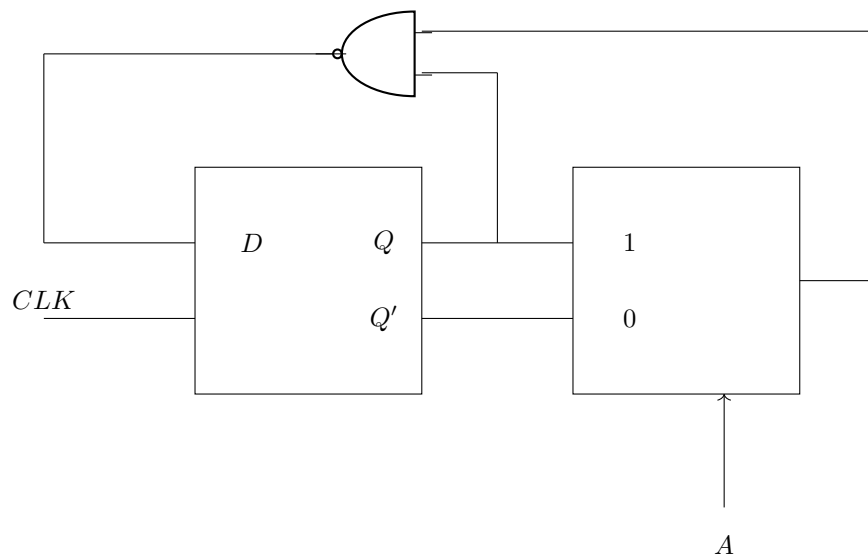
Q.39. The state transition diagram for the circuit shown is




1. (A)

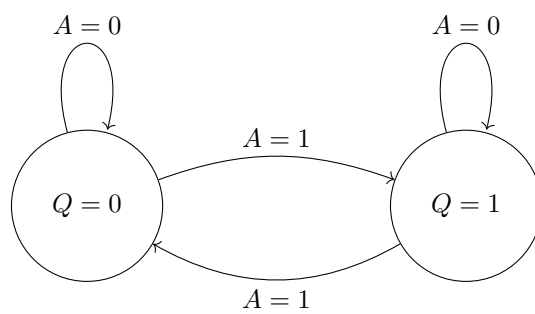


2. (B)

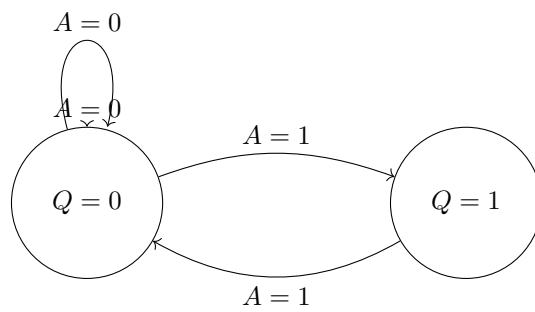

3. (C)

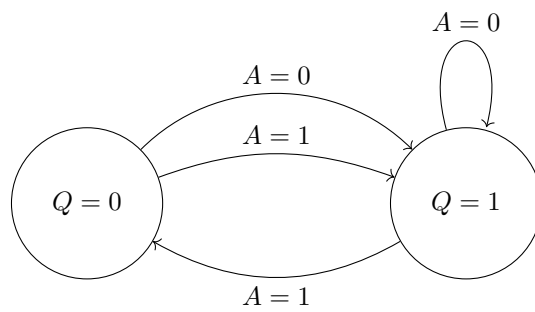

4. (D)

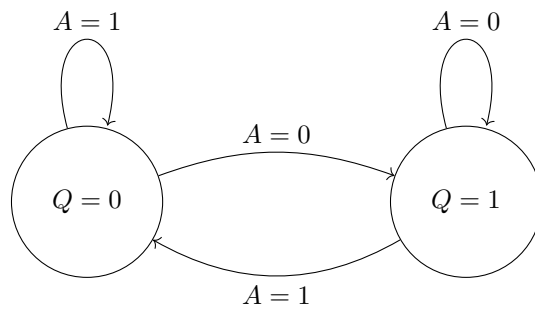

2 Components

Component	Values	Quantity
ArduinoUNO		1
JumperWires	M-M	10
Breadboard		1
LED		1
Resistor	220ohms	1

3 Reduction of logical circuit

The output of 2:1 mux is P.

Now , $P = AQ + A'Q'$

$$D = (Q.P)'$$

$$D = (Q(AQ + A'Q'))'$$

$$D = (A(Q.Q) + (A'Q'Q))' \quad D = (AQ)'$$

The equation after reducing the logical circuit is:

$$D = (AQ)'$$

4 Truth table

Q	A	Q'	Input(D)	Clock	Next State(Q+)
0	0	1	1	↑	1
1	0	0	1	↑	1
1	1	0	0	↑	0
0	1	1	1	↑	1

5 Next stages

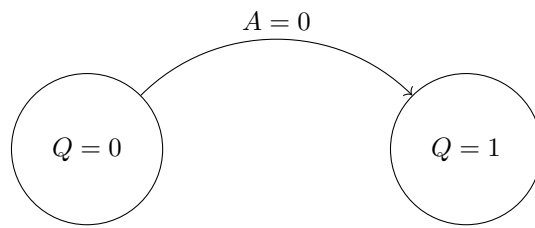


Figure 1: Stage 1

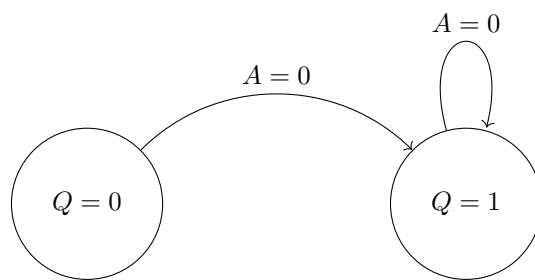


Figure 2: Stage 2

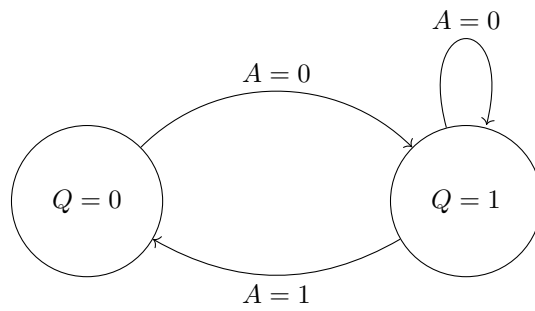


Figure 3: Stage 3

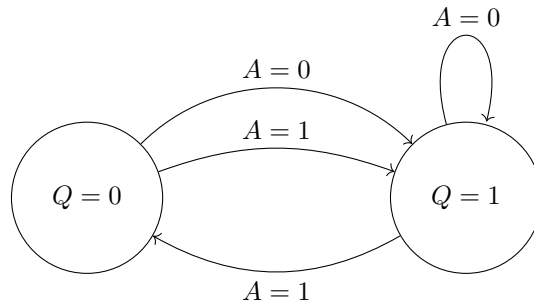


Figure 4: Stage 4

6 implementation

Arduino pin	INPUT	OUTPUT
2	Q	
3	A	
8		D

7 Procedure

1. Connect the circuit as per the above table.
2. Connect the Output pin D to the LED.
3. Connect the other end of the LED to the Ground terminal.
4. Connect inputs to Vcc for logic 1, ground for logic 0.
5. Execute the circuits using the below code.

<https://github.com/madhu-addanki/FWC/tree/main/vaman/fpga/code>

6. Change the values of Q and A in the code and verify the Truth table .